

Minor Project

Multiplexer and Demultiplexer Design

- **Objective:** Design a 2:1 multiplexer (MUX) and a 1:2 demultiplexer (DEMUX) using VHDL. Simulate the functionality of both designs to understand how data selection and routing work.
- **Features:**
 - Design a 2:1 multiplexer (MUX) and implement its functionality.
 - Design a 1:2 demultiplexer (DEMUX) and demonstrate data distribution.
 - Simulate both designs using ModelSim.
- **Tools:** VHDL for design, ModelSim for simulation.